

Phantom power feedthrough circuit to allow using a non-phantom powered processor with a phantom powered microphone powered by a phantom powered input. In this case, the non-phantom device was a Digitech vocal processor. It was not feasible to patch this device via the mixer's channel inserts.

